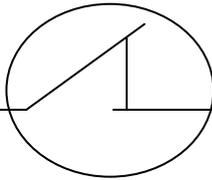


Input Protection:

- 1) Fuse
- 2) MCB
- 3) RCBO – The use of an RCBO will depend on leakage current



Thermal Limit Switch

Mounted on the Power Resistor or on its heat sink. NC - opens when temperature is exceeded



Power Resistor:

See comments to the right hand side

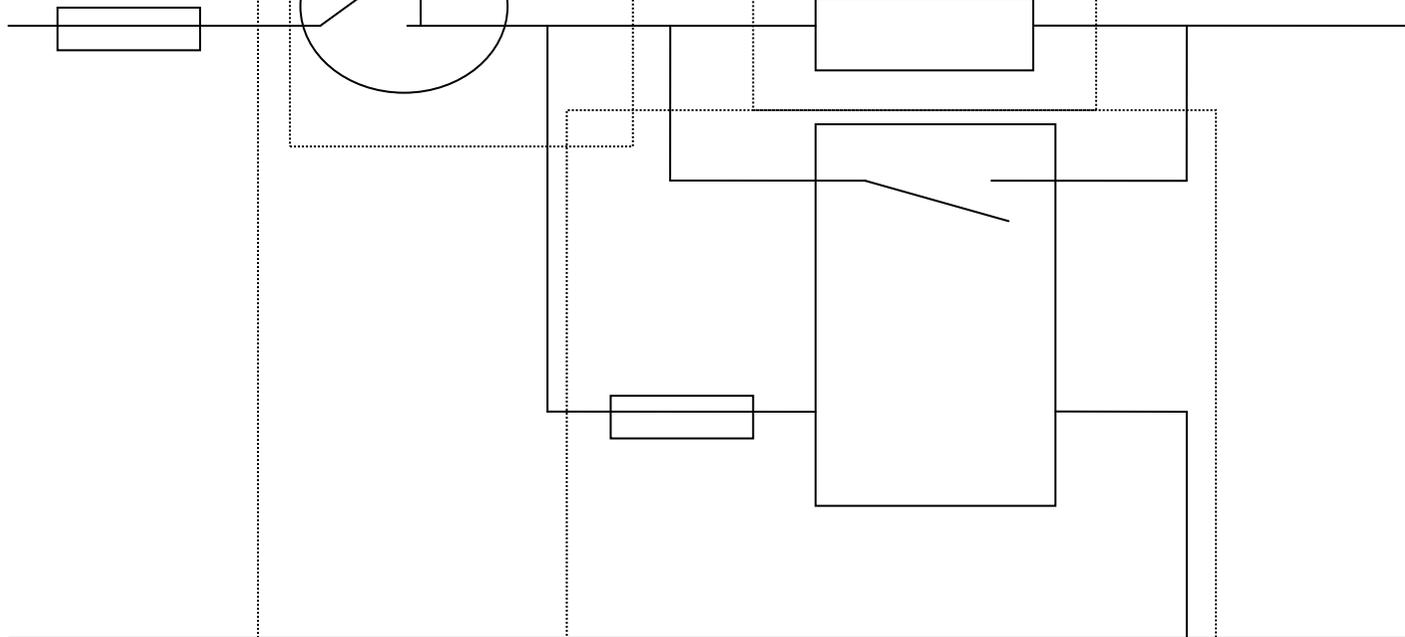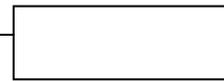

Timer Relay:

Rated for at least 1.5X running current, closes after X amount of time based upon the setting.

Aux contact can be used for an enable signal for electronics further up. If a Mains rated coil ensure that a fuse is used to protect it.

Power Resistor:

Calculations:

Power ignoring Power factor:

$$P = \sqrt{2} \times V \times I$$

$$P = I \times I \times R$$

$$V_{pk} = \sqrt{2} \times V$$

$$V = I \times R$$

So to limit current to say 3A inrush, with a 230V supply:

$$\frac{230 \times \sqrt{2}}{3} = 108.4 \text{ ohms}$$

$P = 965W$ remember that while this is a big power resistor it will limit the peak inrush current very effectively – when looking at ratings remember that most power resistors have high rating for the few seconds you require if mounted to a heat sink, or designed as power resistors.

You must ensure that you supply enough current to the transformer for it to magnetise correctly.